



# FOUNTAIN UNIVERSITY, OSOGBO, NIGERIA.

P.M.B.4491, OSOGBO, OSUN STATE.

COLLEGE OF NATURAL AND APPLIED SCIENCES

DEPARTMENT OF MATHEMATICAL AND COMPUTER SCIENCES

2021/2022 FIRST SEMESTER EXAMINATION

CPS 205: COMPUTER HARDWARE

Credit Unit/Status: 2 (C)

Time Allowed: 2.00Hours.


22/03/2022

INSTRUCTION(s): ATTEMPT ALL QUESTIONS IN SECTION A AND ONLY ONE (1) QUESTION IN SECTION B.

## SECTION A

### Question 1

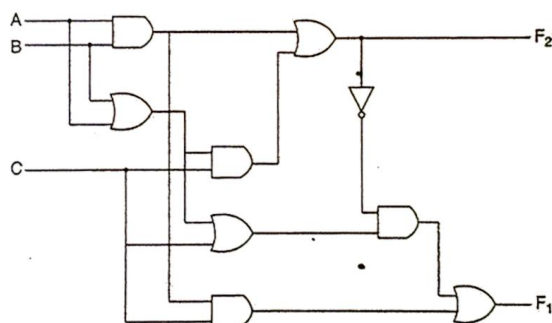- a) Explain the following terms in relation to Computer Hardware Design. [12½marks]
- (i) Logic Gates. (ii) Integrated Circuits. (iii) Combinational Circuits  
(iv) Sequential Circuits (v) Karnaugh maps.
- b) Enumerate the types of Integrated Circuits and their applications. [5marks]
- c) Why must System Designer strive to build less complex circuits? [2 ½ marks]
- d) Analyze the two-output combinational circuits shown in Figure below.
- (i) Derive the truth table of the circuit and obtain the Boolean functions for the two outputs (F1 & F2) of the circuit operation. [4marks]



- (ii) Find the value of F1 and F2 if A =1, B=0 and C=1. [1mark]

### Question 2

- a) Write short note on the following devices: [12 ½ marks]
- (i) Peripheral devices (ii) Printers (iii) Primary Memory  
(iv) Magnetic devices (v) Character recognition device.
- b) Among the selling points of microcomputers are:
- (i) The size of the RAM;  
(ii) The speed of the processor.  
(iii) The size of the hard disk.

Write an essay of not more than 70 words to justify each of the selling points.

[5marks]

- c) Highlight the factors to consider when you want to buy an appropriate printer. [2 ½ marks]

## SECTION B

### *Question 1*

- a) Assuming the FUO management is planning to install an Alarm Bell in the Server room, to protect it from unauthorized entry. The sensor device provides the following logic signal: C= 1 when the Control system is active; D = 1 if the Door is closed; M=1 if there is a Motion in the room; and Q = 1 if the motion is open to the public. Design a digital circuit that will be used to control the Alarm bell. [5marks]  
[10marks]
- b) Differentiate between the following devices:
- Primary and Secondary Storage.
  - Hard disks and Magnetic Tapes.
  - DRAM and MPUs.
  - Combinational circuits and Sequential circuits.
  - Laser and Inkjet printers.

### *Question 2*

- a) With the aid of an illustration, describe how Computer components interact to make a functional computing system. [5marks]
- b) A 4-bit binary number is applied to a circuit on four lines **A, B, C, and D**. The circuit has a single output, '**O**', which is true if the number is in the range 3-12, inclusive.
- Draw a truth table for this problem, and obtain a simplified expression for **O** in terms of the inputs. [8marks]
  - Implement the circuits in terms of logic gates. [2marks]